

Basic Low Noise Amplifier design and implementation

50 MHz and up, March 2020,


Goran Popovic AD6IW

Amplifiers are designed for:

- Gain
- Low noise
- Wideband
- Power
- Efficiency
- Linearity
- All above have different design procedure and requirements

Select part and start with S parameters

GRAPHICAL VIEW OF S-PARAMETERS

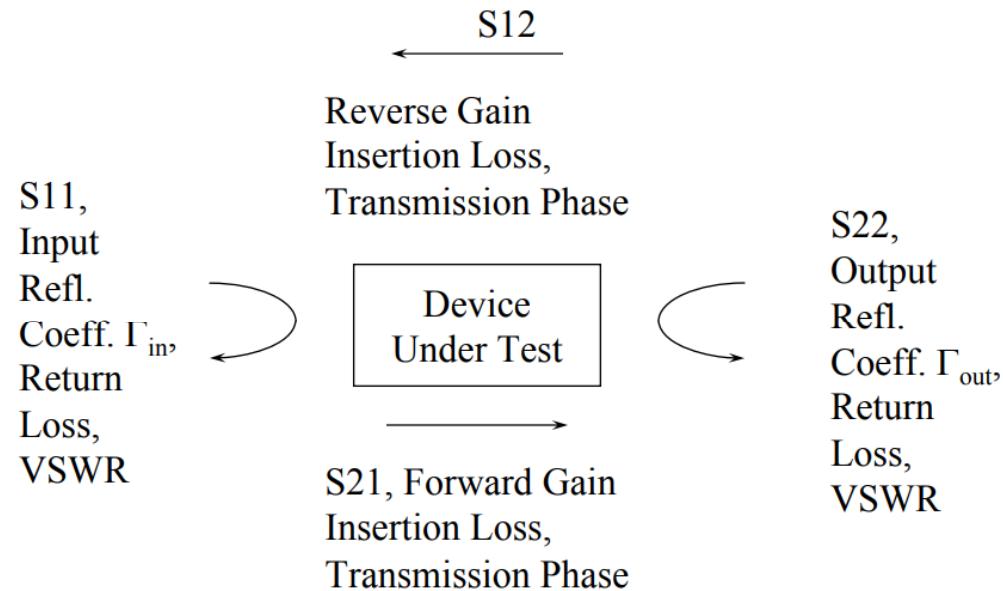

Touchstone s2p file, and noise parameters

```

! NEC Compound Semiconductor Devices Ltd.
! 22. July 2005
! NE3512S02
! VD = 2 ID = 10 mA
# GHz S MA R 50
! f S11 S21 S12 S22
! GHz MAG ANG MAG ANG MAG ANG MAG ANG
2.000 0.972 -24.000 4.722 152.300 0.025 73.300 0.647 -17.900
2.500 0.960 -30.200 4.685 145.500 0.031 68.900 0.638 -22.400
3.000 0.945 -36.300 4.687 138.600 0.036 65.000 0.633 -26.600
3.500 0.927 -42.300 4.670 131.900 0.042 60.900 0.622 -31.300
4.000 0.907 -48.500 4.655 125.100 0.048 56.500 0.613 -35.800
4.500 0.884 -55.300 4.624 118.000 0.053 52.800 0.601 -39.600
5.000 0.860 -61.000 4.615 109.900 0.058 48.800 0.587 -46.000
5.500 0.837 -68.000 4.574 104.300 0.063 44.300 0.569 -49.000
6.000 0.808 -74.900 4.542 97.400 0.068 41.100 0.553 -52.600
6.500 0.780 -81.900 4.506 90.500 0.073 36.600 0.535 -57.400
7.000 0.752 -88.600 4.463 83.600 0.077 32.800 0.512 -61.600
7.500 0.720 -95.500 4.416 76.800 0.081 29.200 0.493 -65.800
8.000 0.687 -103.000 4.367 69.900 0.086 25.800 0.474 -70.400
8.500 0.664 -110.600 4.315 63.000 0.089 21.600 0.448 -74.500
9.000 0.630 -117.900 4.252 56.200 0.092 17.900 0.424 -77.700
9.500 0.596 -126.000 4.167 49.600 0.095 14.900 0.401 -81.700
10.000 0.573 -133.400 4.134 43.200 0.099 11.400 0.382 -86.700
10.500 0.552 -141.900 4.078 36.400 0.102 8.300 0.355 -90.800
11.000 0.531 -150.300 4.010 29.800 0.105 4.800 0.330 -95.500
11.500 0.507 -158.900 3.959 23.200 0.109 1.900 0.305 -101.000
12.000 0.495 -168.300 3.885 16.400 0.112 -1.400 0.280 -105.000
12.500 0.475 -177.300 3.835 10.000 0.115 -4.400 0.251 -111.100
13.000 0.469 -173.600 3.763 3.800 0.117 -7.200 0.229 -116.600
13.500 0.458 -165.500 3.701 -2.600 0.121 -10.500 0.204 -123.000
14.000 0.452 -154.200 3.644 -9.300 0.124 -14.100 0.176 -130.400
14.500 0.454 -145.200 3.583 -15.600 0.128 -17.000 0.152 -140.900
15.000 0.456 -135.700 3.519 -22.200 0.131 -20.600 0.127 -152.400
15.500 0.458 -126.700 3.460 -28.600 0.134 -23.800 0.108 -168.900
16.000 0.463 -116.300 3.395 -35.200 0.137 -27.100 0.107 168.400
16.500 0.485 -107.900 3.325 -41.600 0.140 -30.400 0.099 147.400
17.000 0.490 -99.200 3.263 -48.200 0.143 -33.900 0.113 125.900
17.500 0.507 -89.900 3.199 -54.700 0.147 -37.900 0.138 109.300
18.000 0.525 81.800 3.129 -61.300 0.149 -41.700 0.161 98.300

! f Fmin Gammaopt Rn/50
! GHz dB MAG ANG -
2.000 0.320 0.866 14.500 0.289
2.500 0.320 0.838 18.800 0.276
3.000 0.320 0.814 23.100 0.264
3.500 0.320 0.793 27.500 0.252
4.000 0.320 0.774 32.000 0.241
4.500 0.320 0.758 36.600 0.229
5.000 0.320 0.742 41.300 0.218
5.500 0.330 0.727 46.100 0.206
6.000 0.330 0.713 51.000 0.194
6.500 0.340 0.699 56.200 0.182
7.000 0.340 0.684 61.500 0.169
7.500 0.350 0.669 67.000 0.156
8.000 0.360 0.654 72.700 0.143
8.500 0.360 0.637 78.700 0.130
9.000 0.370 0.619 84.900 0.116
9.500 0.390 0.601 91.300 0.103
10.000 0.400 0.581 98.100 0.090
10.500 0.410 0.561 105.100 0.078
11.000 0.420 0.539 112.500 0.067
11.500 0.440 0.517 120.200 0.056
12.000 0.450 0.495 128.200 0.047
12.500 0.470 0.472 136.600 0.040

```

Gsource_max = $1/(1-S11)^2$ 1.43dB

Gload max = $1/(1-S221)^2$ 1.22dB

$Go = [S21]^2$ 11.54dB

Gtu max = $1.43 + 1.22 + 11.54 = 14.19$ dB

MSG = $S21 / S12$ 16.01dB


Basic amplifier design steps

- Amplifier max. gain design, unilateral $S_{12} = 0$, or bilateral conjugate match
- Stability circle, amplifier must be unconditional stable.
- Find optimum impedances for desired Gain,
Gamma opt. for low Noise Figure, and Gamma load.
- Match device with appropriate network circuits.
- Optimize LNA, it is trade off between NF, Gain, and Stability.
- Design LNA with S parameters and set of equation's, is tedious and time consuming but it is necessary to understanding design procedure.
- Computer simulation software, save time and get better results

Basic equations, conjugate gain amplifier approach


Design Equations Using S-Parameters	
Eq	Remarks
(1) $MSG_{dB} = 10 \log \left \frac{S_{21}}{S_{12}} \right $	max. stable gain
(2) $D = (S_{11} S_{22}) - (S_{12} S_{21})$	
(3) $K = \frac{1 + D ^2 - S_{11} ^2 - S_{22} ^2}{2 S_{12} S_{21} }$	Stability Factor
(4) $B_1 = 1 + S_{11} ^2 - S_{22} ^2 - D ^2$	
(5) $MAG_{dB} = MSG_{dB} + 10 \log (K \pm \sqrt{K^2 - 1})$	Use minus before radical positive, and plus when
(6) $C_1 = S_{11} - (D \times S_{22}^*)$	S_{22}^* = conjugate of S_{22}
(7) $ \Gamma_{in} = \left[\frac{B_1 \pm \sqrt{B_1^2 - 4 C_1 ^2}}{2 C_1 } \right]$	Use minus before radical positive, and plus when
(8) $B_2 = 1 + S_{22} ^2 - S_{11} ^2 - D ^2$	
(9) $C_2 = S_{22} - (D \times S_{11}^*)$	S_{11}^* = conjugate of S_{11}
(10) $ \Gamma_{out} = \left[\frac{B_2 \pm \sqrt{B_2^2 - 4 C_2 ^2}}{2 C_2 } \right]$	Use minus before radical positive, and plus when
(11) $\Gamma_{in} = \Gamma_{in} / \theta C_1$	
(12) $\Gamma_{out} = \Gamma_{out} / \theta C_2$	
$\Gamma_S = \left[S_M + \frac{S_{12} S_{21} \Gamma_L}{1 - (\Gamma_L \cdot S_{22})} \right]^\circ$ Design To <ul style="list-style-type: none"> o change S_M 	

Stability, Gain, NF circles simulation

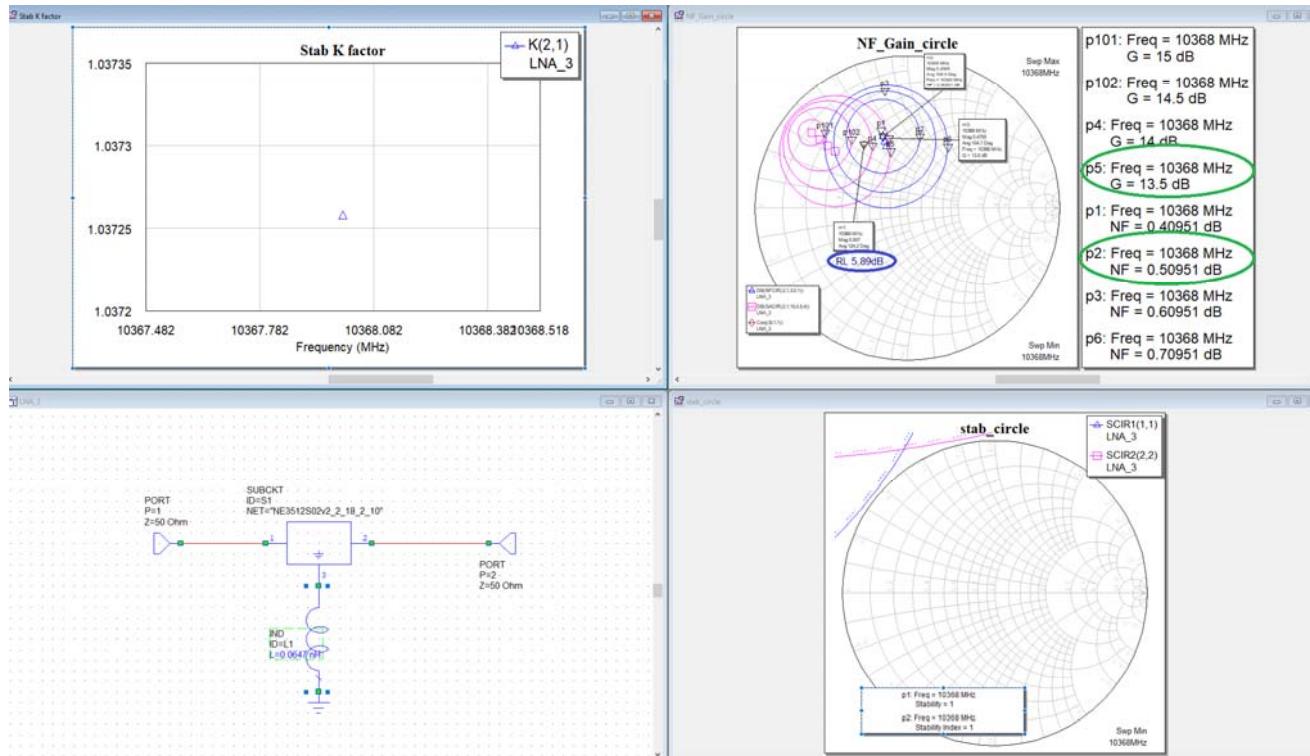

Load pull stability method

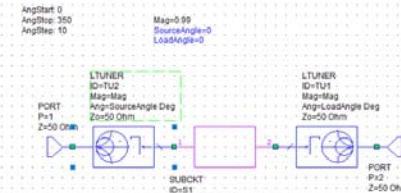Rotate amplifier load around edge of smith chart and check device stability vs. frequency
Tune "LoadAngle" and "Source Angle" from 0 to 360 and check that the measurement is always less than 1
Enable the "LoadAngle" and "Source Angle" sweeps to see the full stability sim



SWPVAR

ID=BaseAngle

VarName="BaseAngle"



values=0.99

SWPVAR

ID=Mag

VarName="LoadAngle"

values=10

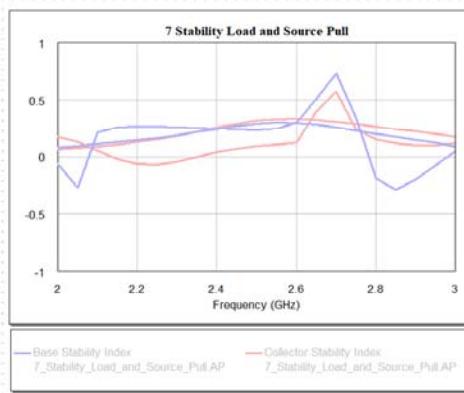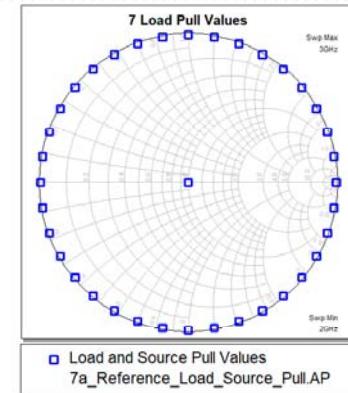

Using Calculator

CALCULATOR INPUTS

Z_o= (ohms)

F= MHz

Source and Load Impedances

Z_S= j

Z_L= j

Source and Load L-Matching Networks

Source: Low Pass High Pass

Load: Low Pass High Pass

S-Parameters (Rectangular Or Polar(Degrees))

S₁₁= -130.5

S₁₂= 26.9

S₂₁= 39.82

S₂₂= -80.19

Starting point

Rollest Stability Factor (K)	
K= <input type="text" value="1.01"/>	
Maximum Allowable Gain	
MAG= <input type="text" value="36.7"/> (Gain) <input type="text" value="15.6"/> (Db)	
Conjugate Input and Output Reflection Coefficients	
GAMA _L <input type="text" value="0.855"/> - <input type="text" value="249"/> (Polar)	
GAMA _S <input type="text" value="0.888"/> + <input type="text" value="213"/> (Polar)	
Input and Output Impedances Looking into Amp	
Z _{SM} <input type="text" value="3.21"/> - <input type="text" value="14.6"/> j	
Z _{LM} <input type="text" value="5.75"/> - <input type="text" value="34.2"/> j	
L-Network Matching Components	
Source	Load
C= <input type="text" value="1.17"/> pf, L= <input type="text" value="0.411"/> nH	C= <input type="text" value="0.852"/> pf, L= <input type="text" value="0.770"/> nH
Q _S = <input type="text" value="3.82"/>	Q _L = <input type="text" value="2.78"/>
<input type="checkbox"/> Parallel leg of L-network near amp	<input type="checkbox"/> Parallel leg of L-network near amp

Equations:

$$D_S = S_{11}S_{22} - S_{12}S_{21}$$

$$K = (1 + |D_S|^2 - |S_{11}|^2 - |S_{22}|^2) / (2|S_{21}||S_{12}|)$$


$$B = 1 + |S_{11}|^2 - |S_{22}|^2 - |D_S|^2$$

$$MAG = |S_{21}|/|S_{21}|(K \pm \sqrt{K^2 - 1}) \rightarrow \text{if } B \text{ is negative use +, otherwise -}$$


Load Reflection Coefficient:

$$GAMA_L$$

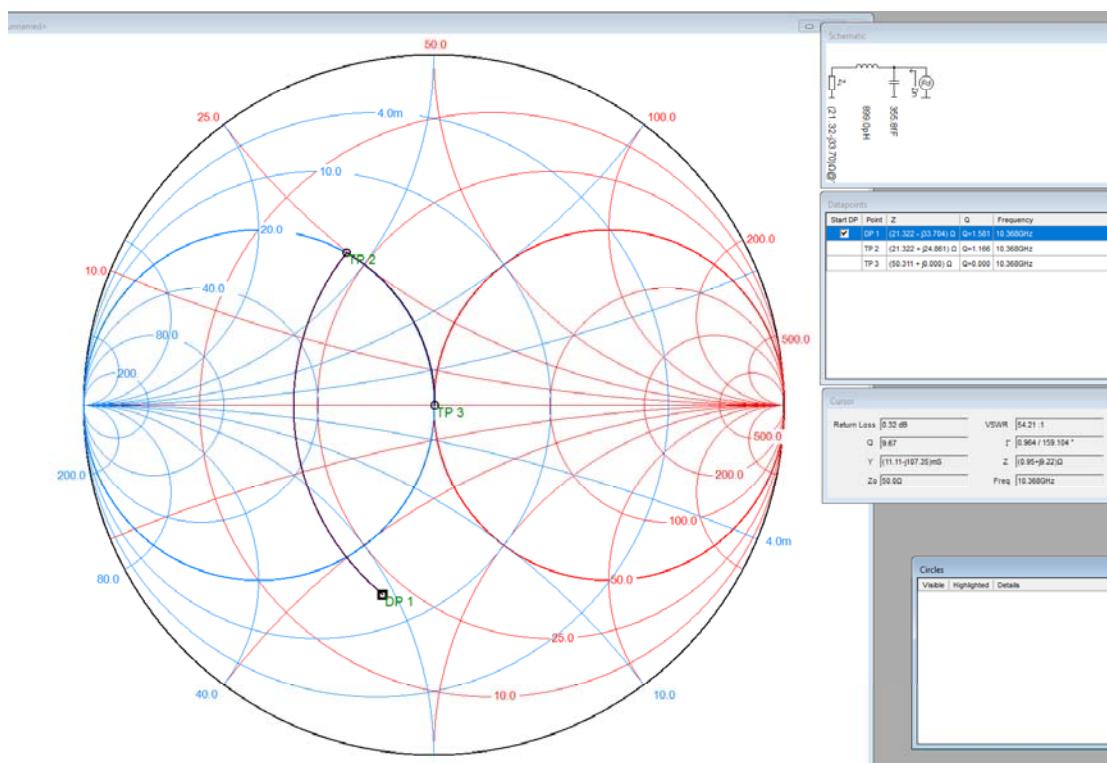
Input matching with ideal lumped elements



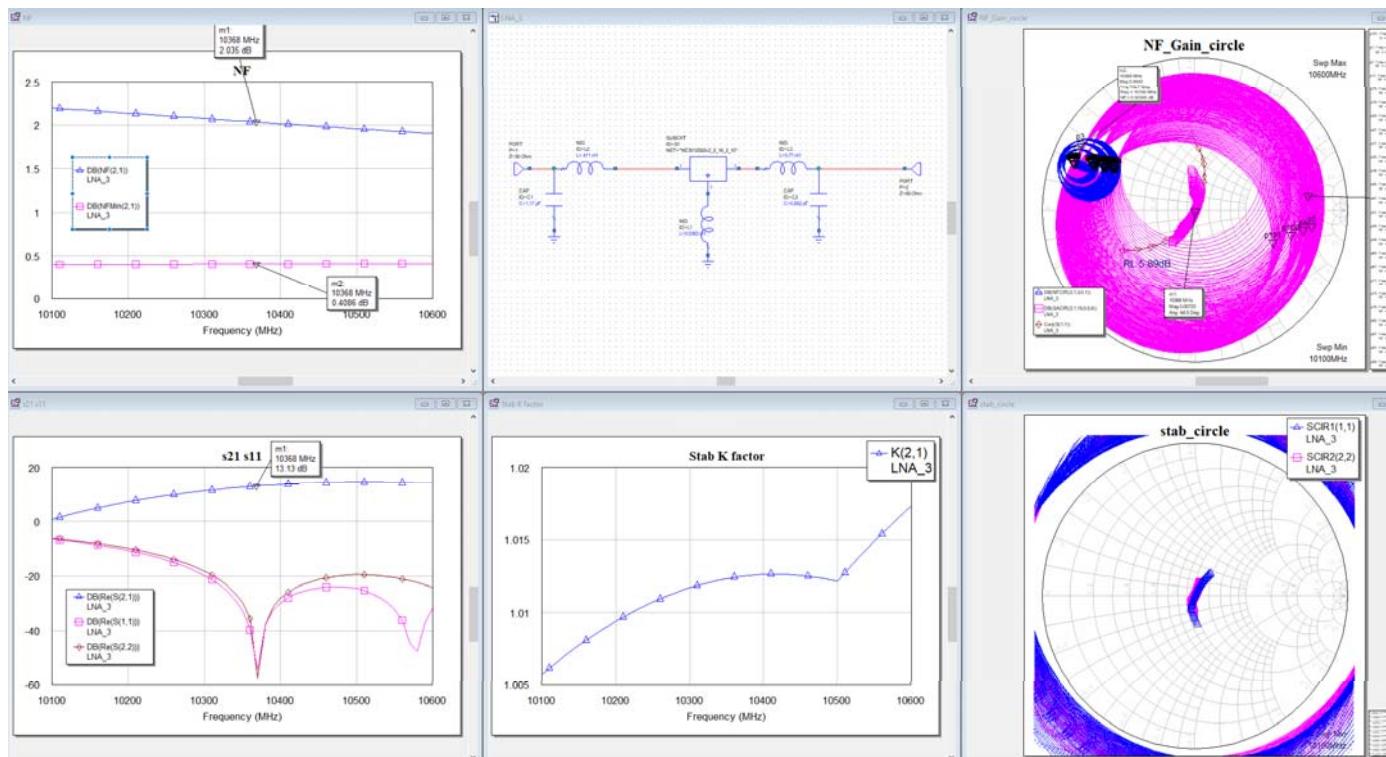
Gain amplifier simulation with ideal lumped components



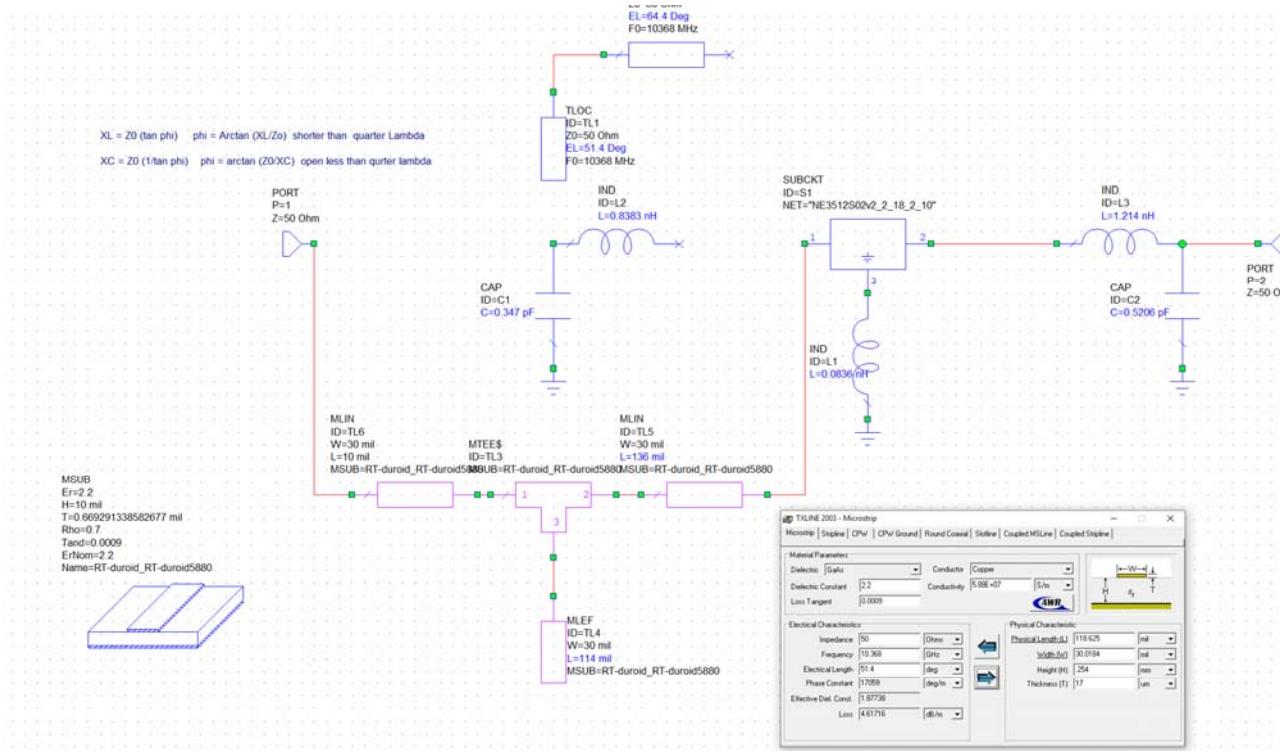Ideal components to Microstrip conversion



Microstrip input matching

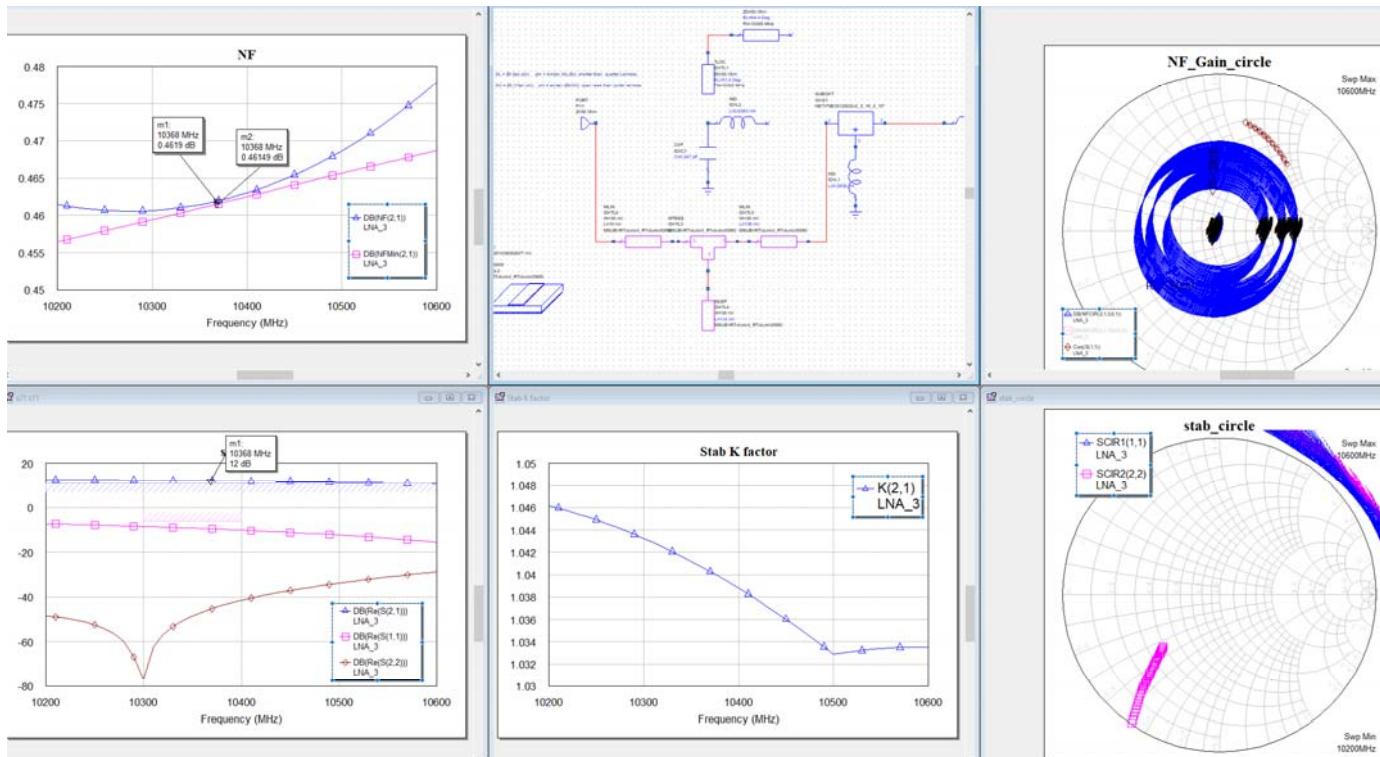

Radial stub Calculator

← → ⌂ flambda.com/stub/stub.php
Apps WE-LQ SMT Induct... E4402B - Keysight /... Filter Wizard | Anal... RF Toc

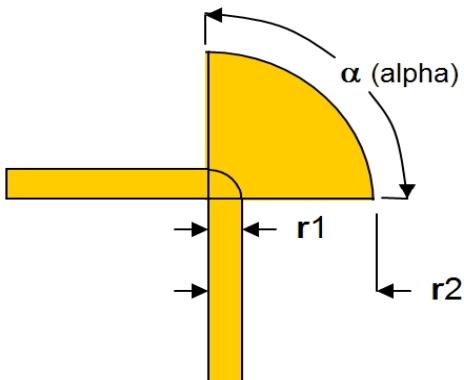


Figure 1. Microstrip Radial Stub

Use the program below to calculate dimension r_2 for a radial stub.
The radial stub is used to provide a broadly resonant RF short circuit.
When cascaded with high impedance quarter-wavelength transmission lines,
the radial stub can provide an effective decoupling network for microwave
amplifiers and other active components.
The range of dielectric constant (ϵ_r) over which the results are valid is 2 to 15.
The frequency range over which the results are valid is 0.3GHz to 30GHz.
The formulas used are the work of Dr. H. A. Atwater of MIT Lincoln Labs, as published in
the November 1985 issue of Microwave Journal.

Units Inches millimeters

Angle alpha 90° 60°

Substrate ϵ_r Dielectric Constant (range 2-15)


Frequency GHz (range 0.3 to 30)

Substrate Height


Radius r_1

r₂= 0.12355766847599 inches

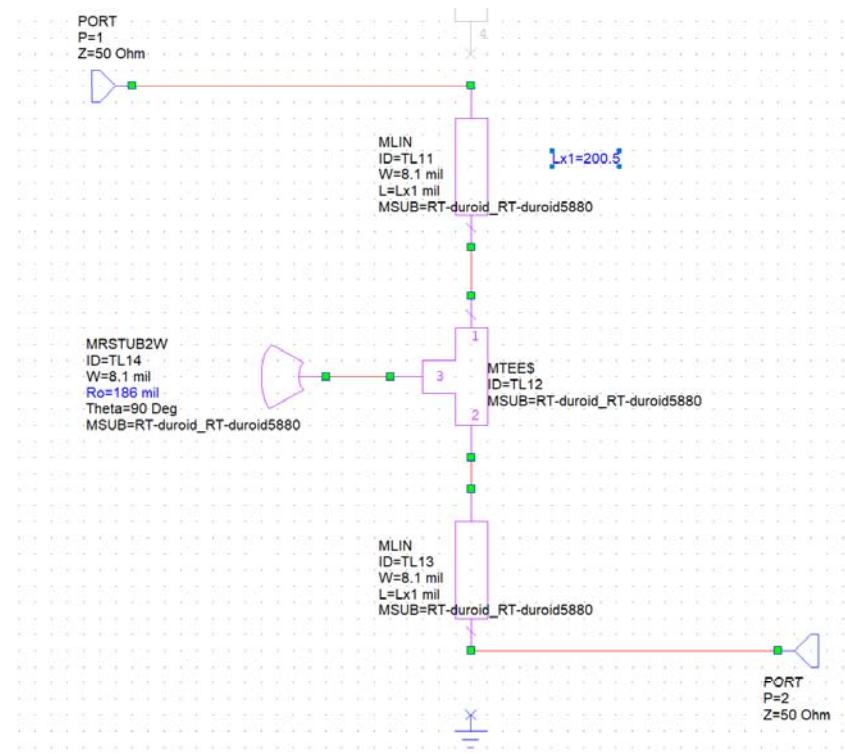
Bias circuit, quarter lambda high impedance microstrip line and radial stub -capacitor




Bias simulation

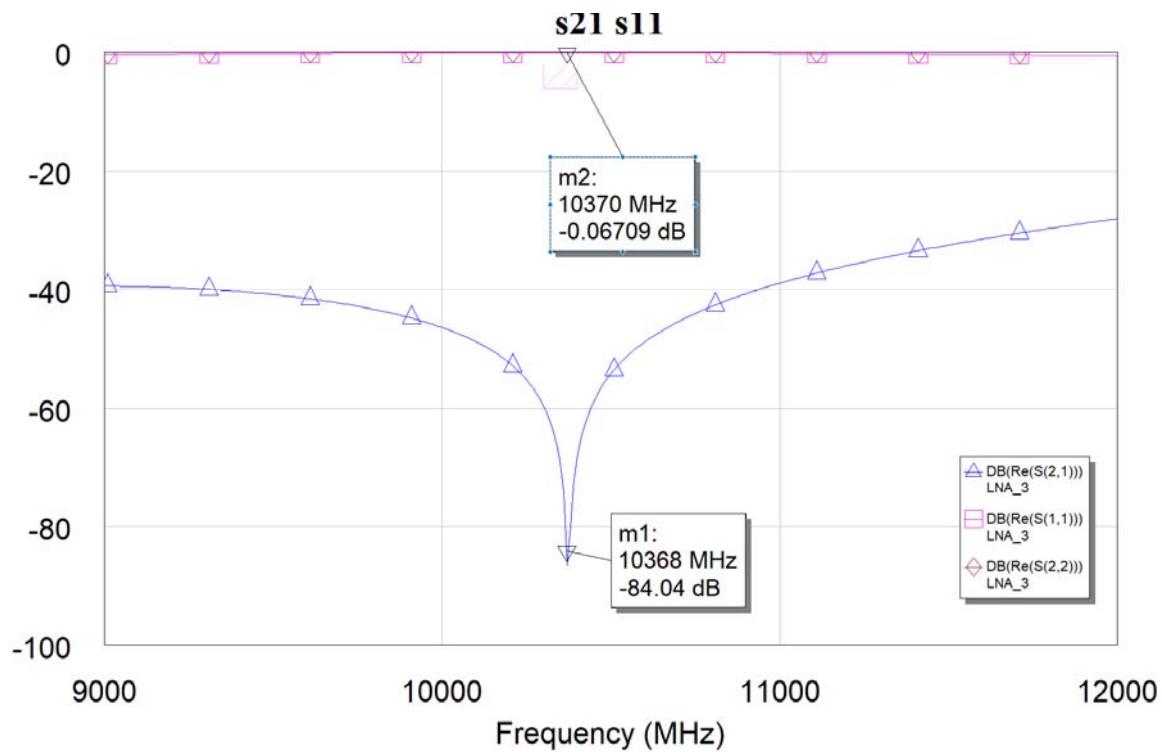

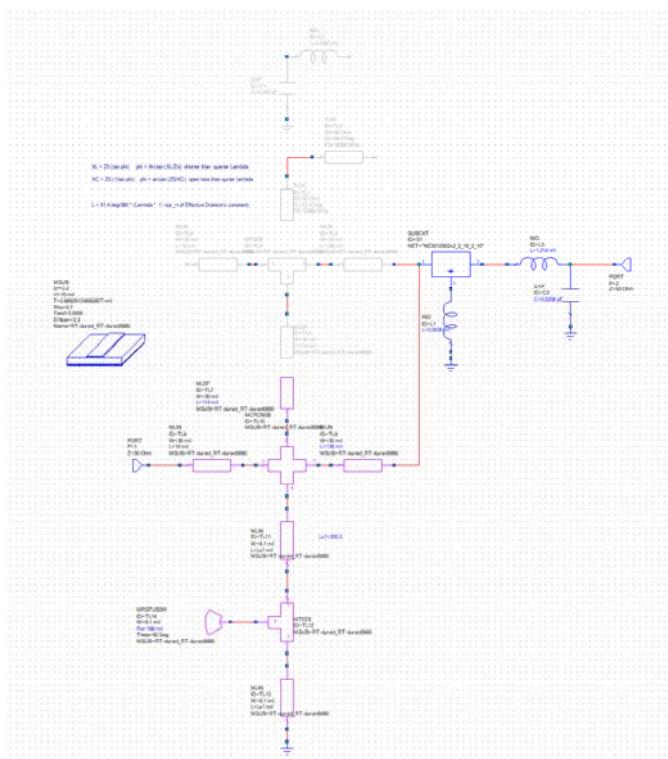Input microstrip matching, bias incorporated




Input matching completed

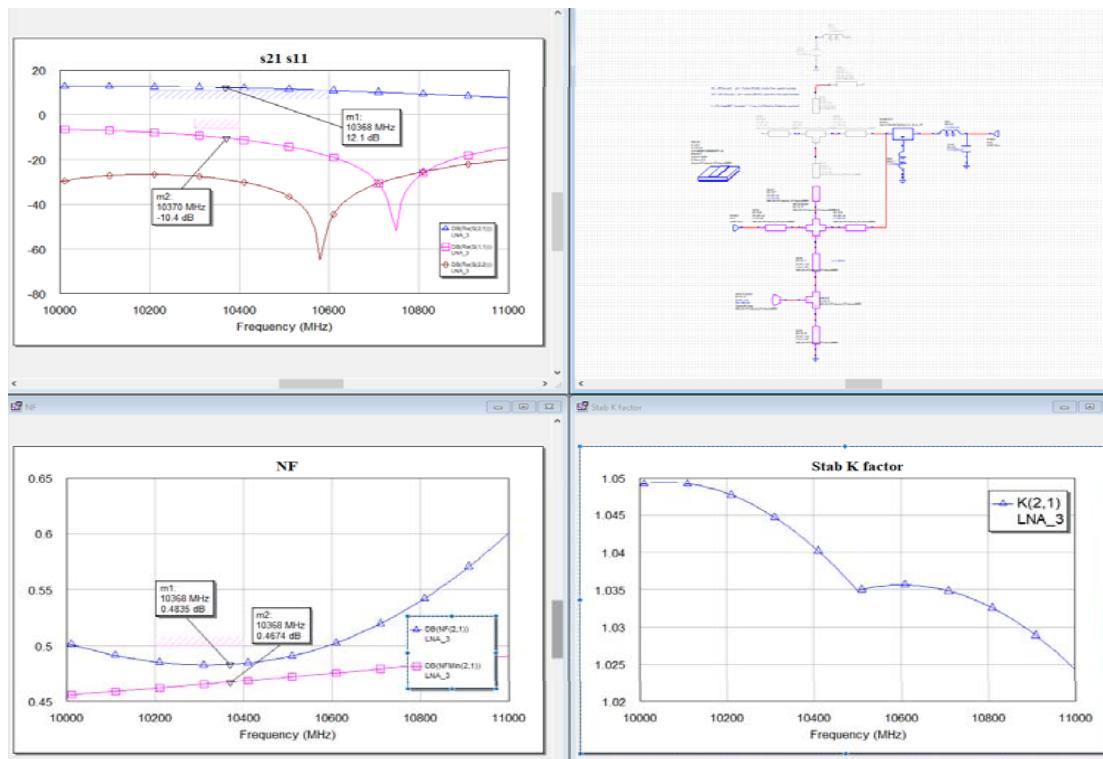


Conjunctive load matching impedance

$$\Gamma_L = \left[S_{22} + \frac{S_{21}\Gamma_s S_{12}}{1 - S_{11}\Gamma_s} \right]_*$$


LNA final schematics

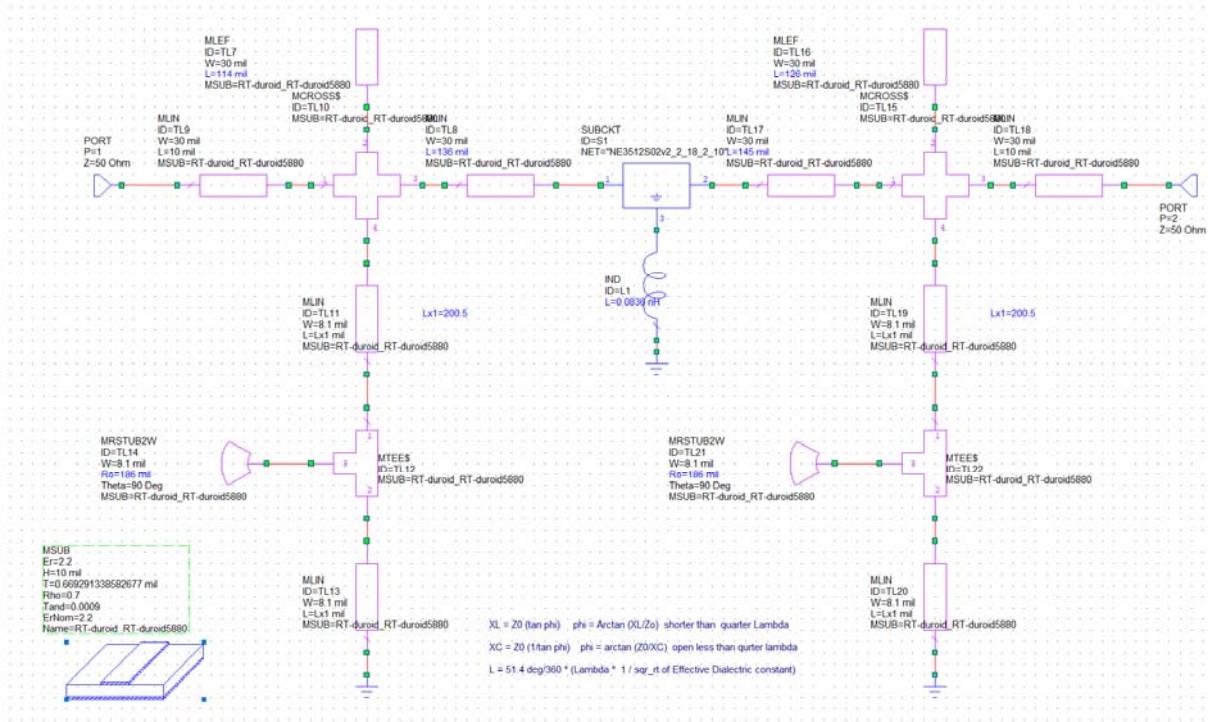

PCB LAYOUT

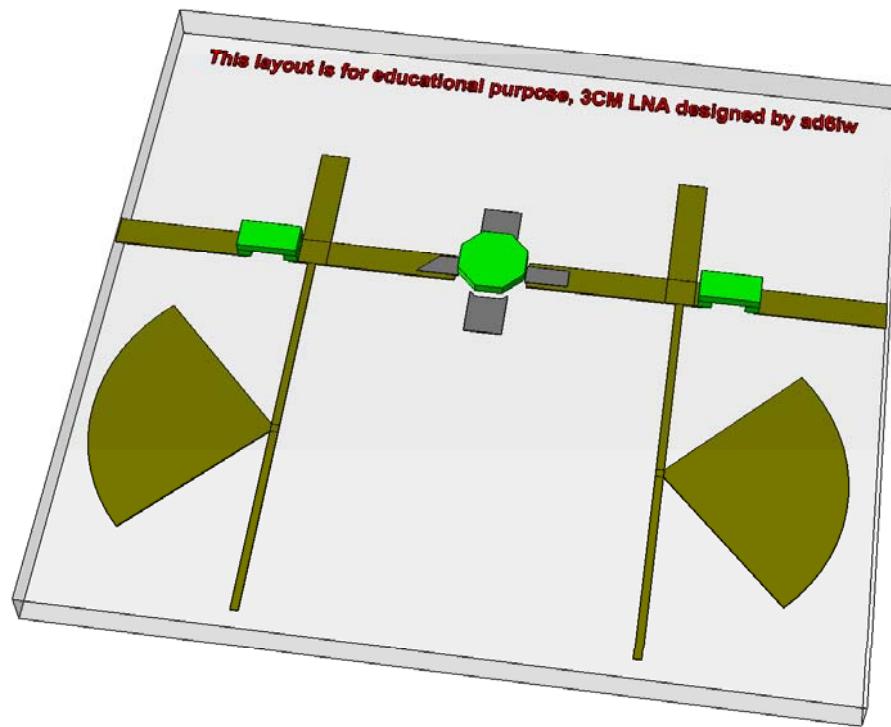


Final simulation results

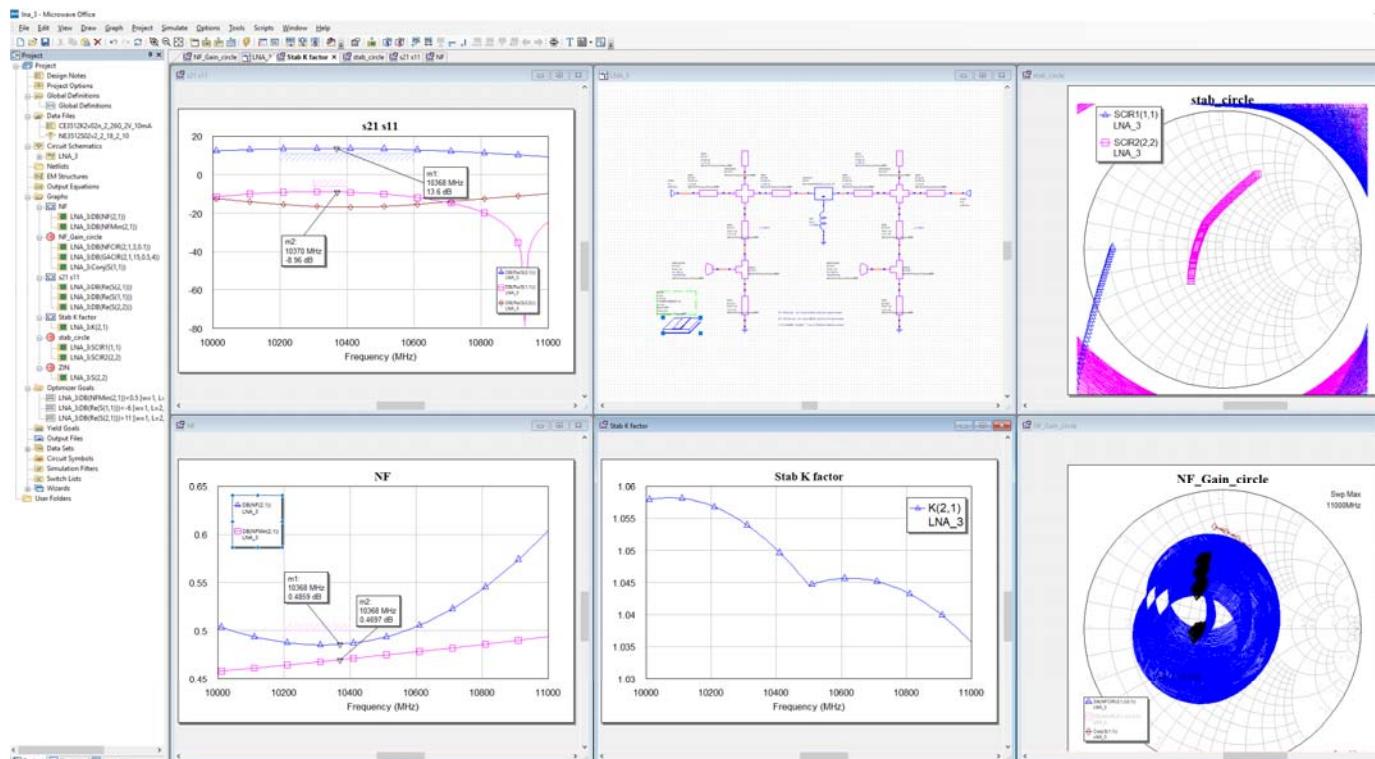

Computer optimization and final steps


- Add coupling capacitors, connectors and optimize again
- EM test, simulate microstrip with substrate and real parts, enclosure eigenmode, cover above traces, connector transition, crosstalk
- Layout and creating Gerber file
- Prototyping
- Testing
- In reality, always lower gain and higher noise figure

LNA Testing and Construction Hints

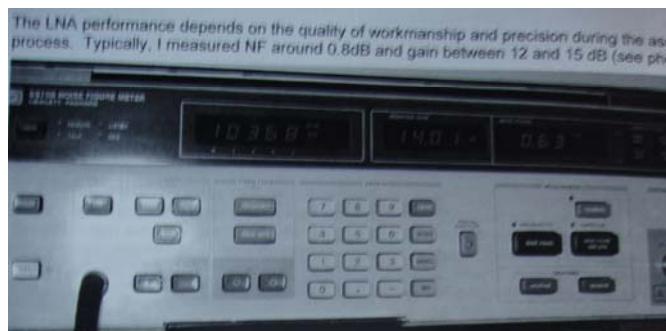


The LNA performance depends on the quality of workmanship and precision during the assembly process. Typically, I measured NF around 0.8dB and gain between 12 and 15 dB (see photo).

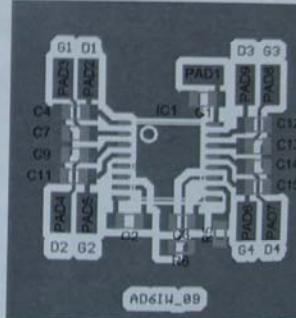The recommended LNA mounting method is with a SMA male connector mounted at the input of the LNA, so the LNA can be connected directly to the SMA transfer relay without an SMA adapter. The insertion loss of an adapter is in the range of 0.1-0.2 dB and it will directly increase the noise figure by that amount.




LNA test with VNA

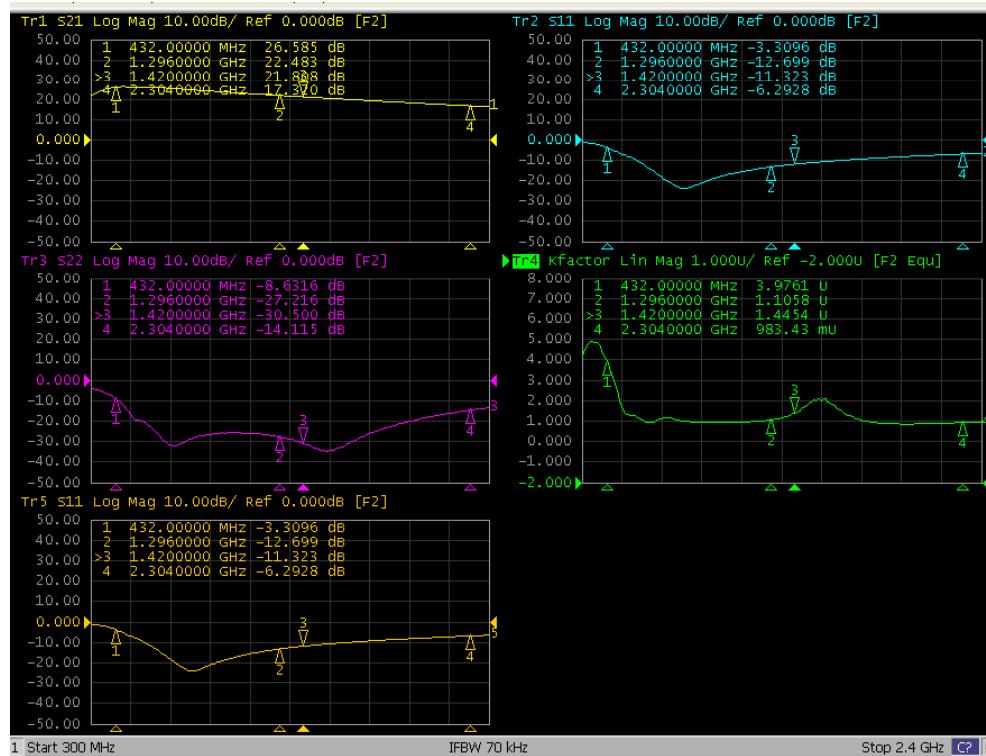

Rollet stability factor, K-factor test with VNA.
This test should be performed with any amp.

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{21}S_{12}|}$$


$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

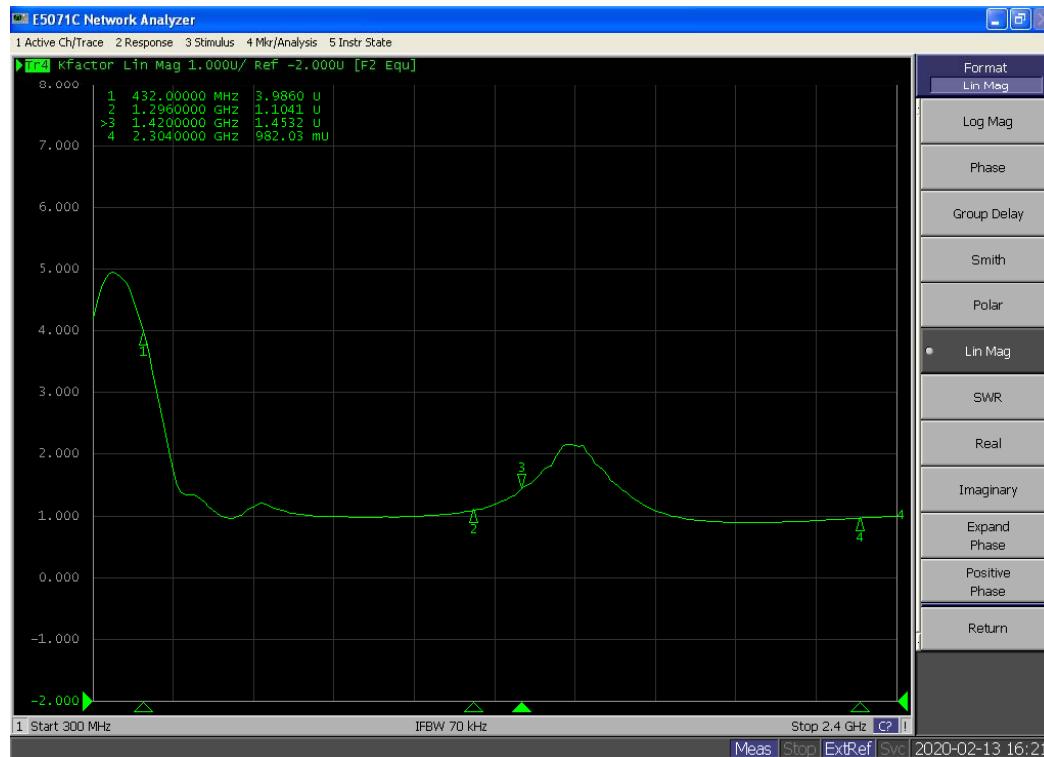


Noise Figure and Gain measurements




3CM LNA schematics

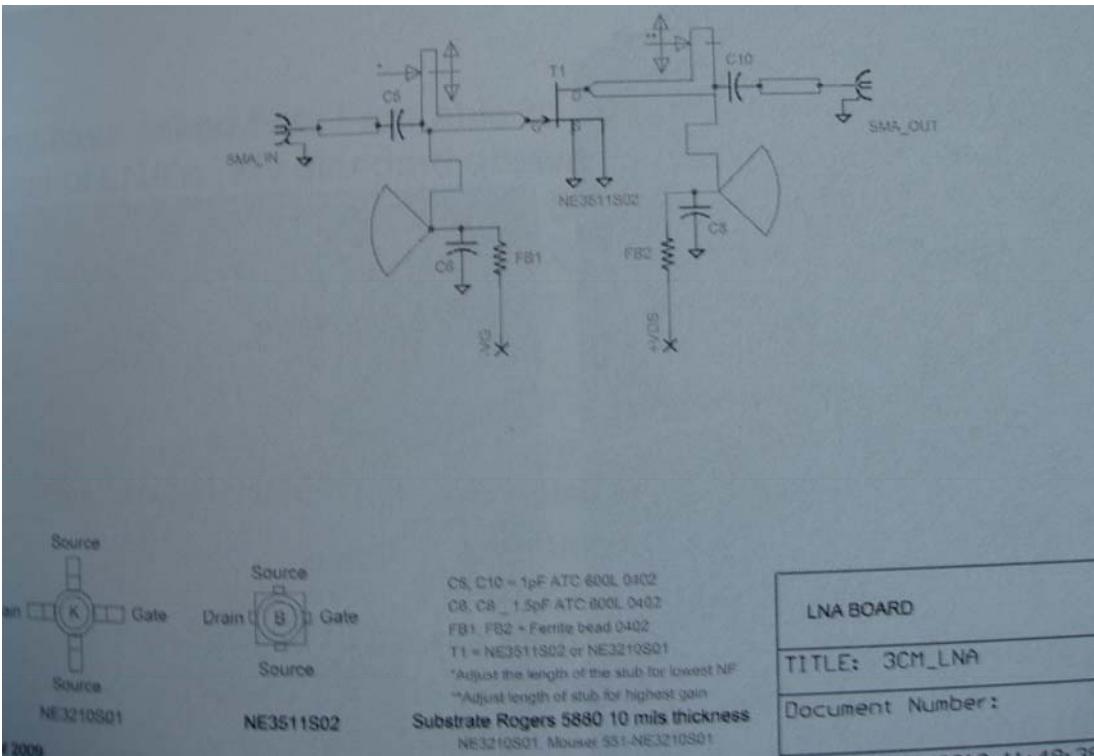


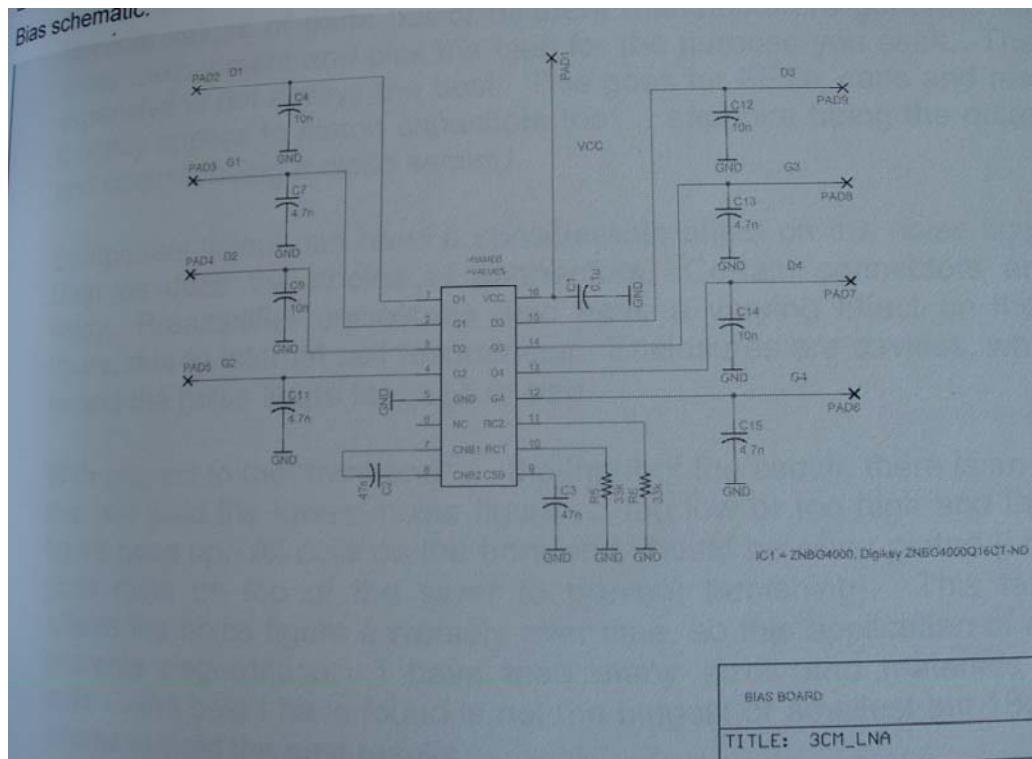
Active Bias circuit, positive and negative voltages for four GaAs Fet's




Layout and enclosure

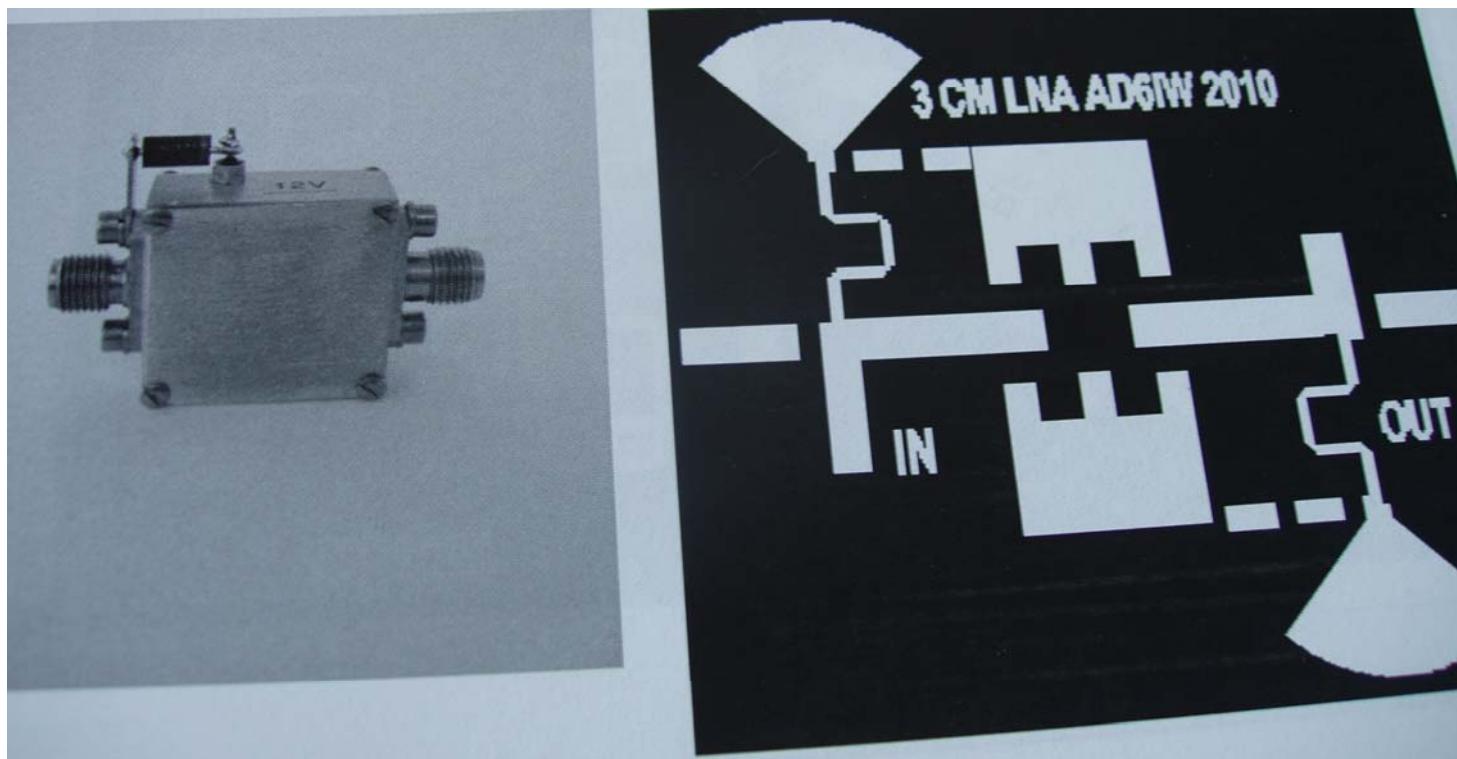


Enclosure and simulation NF

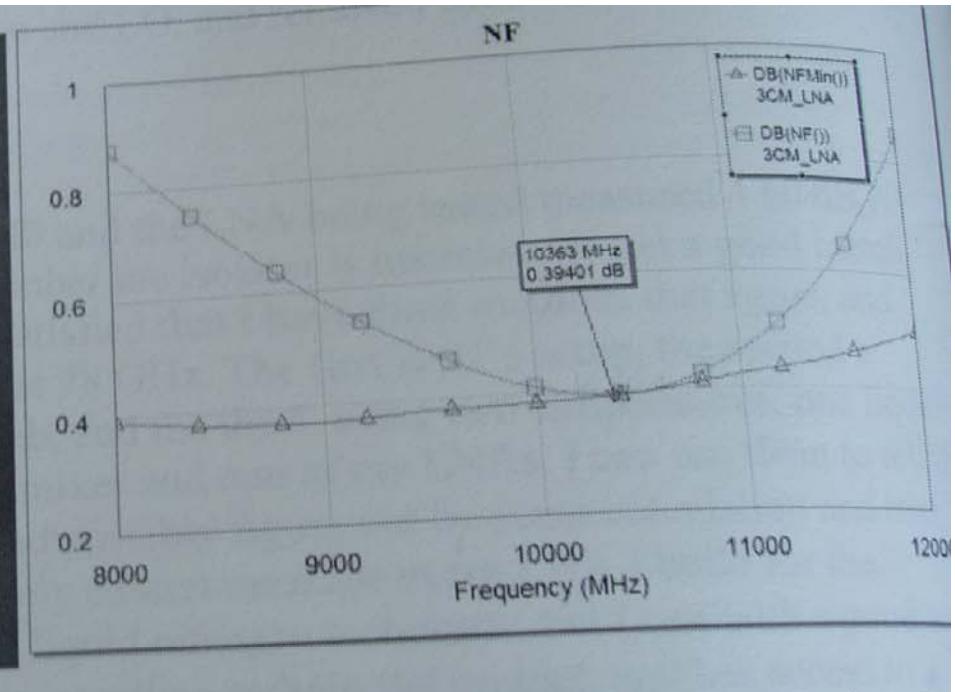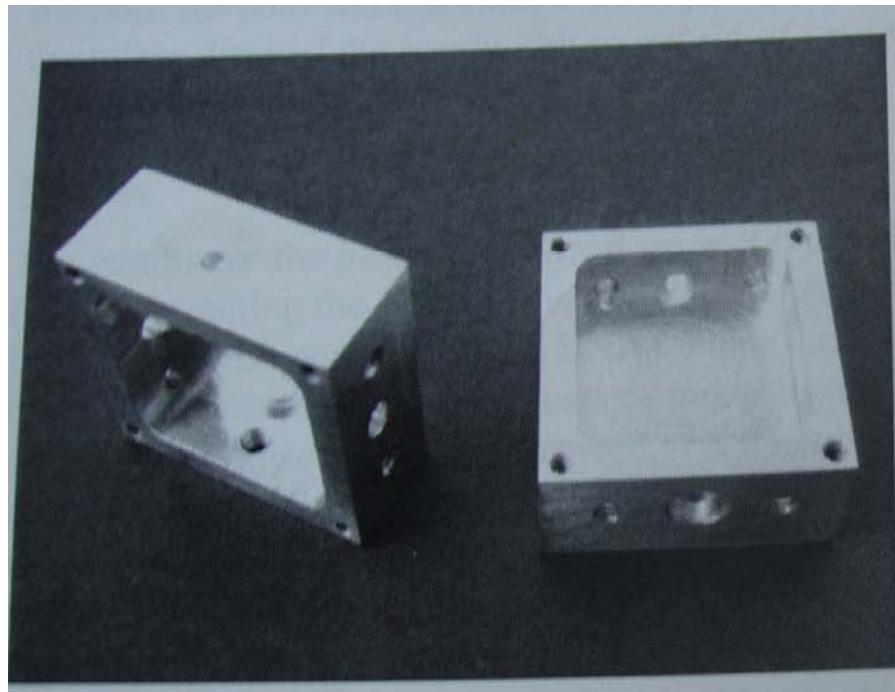

Assembling process

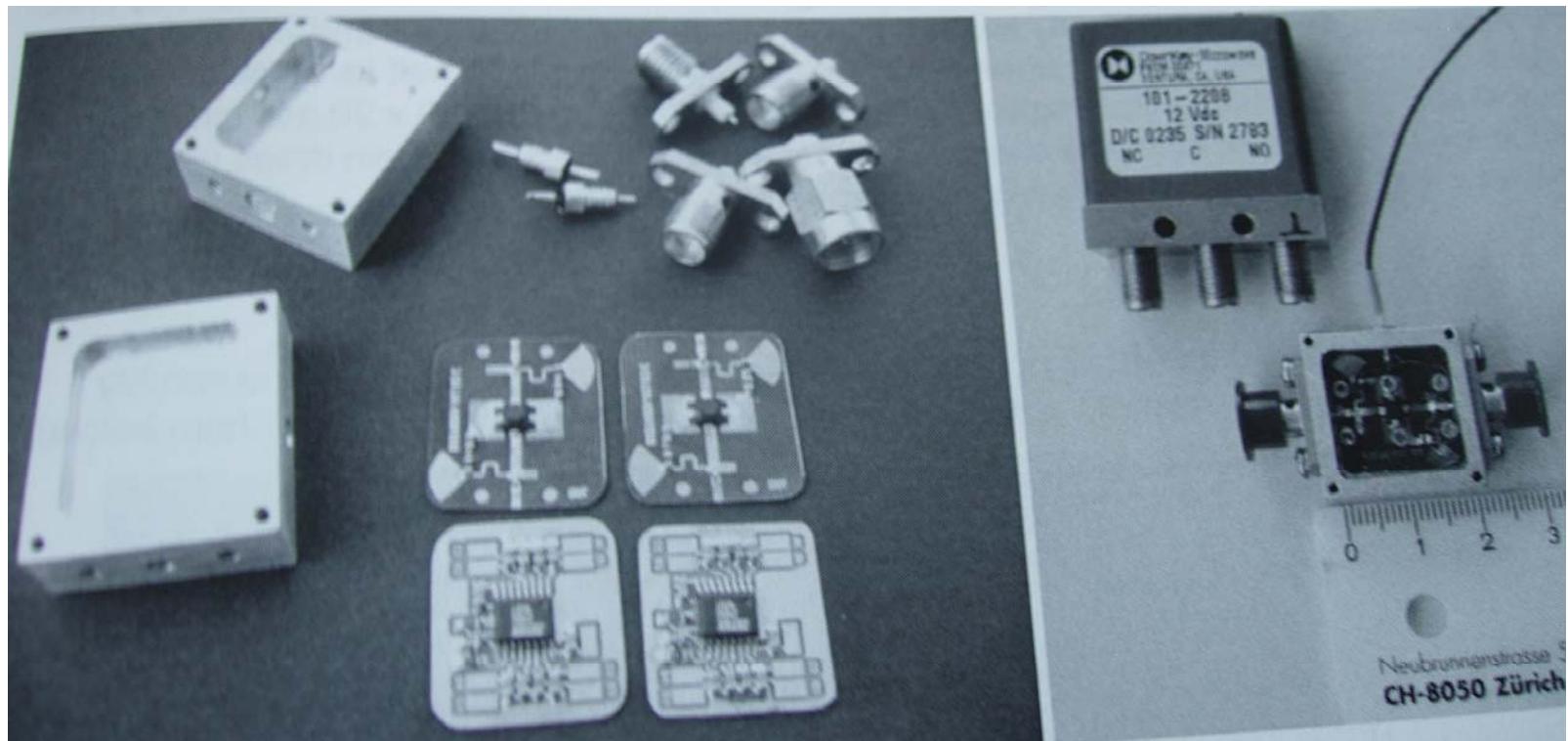

Homebrew LNA's

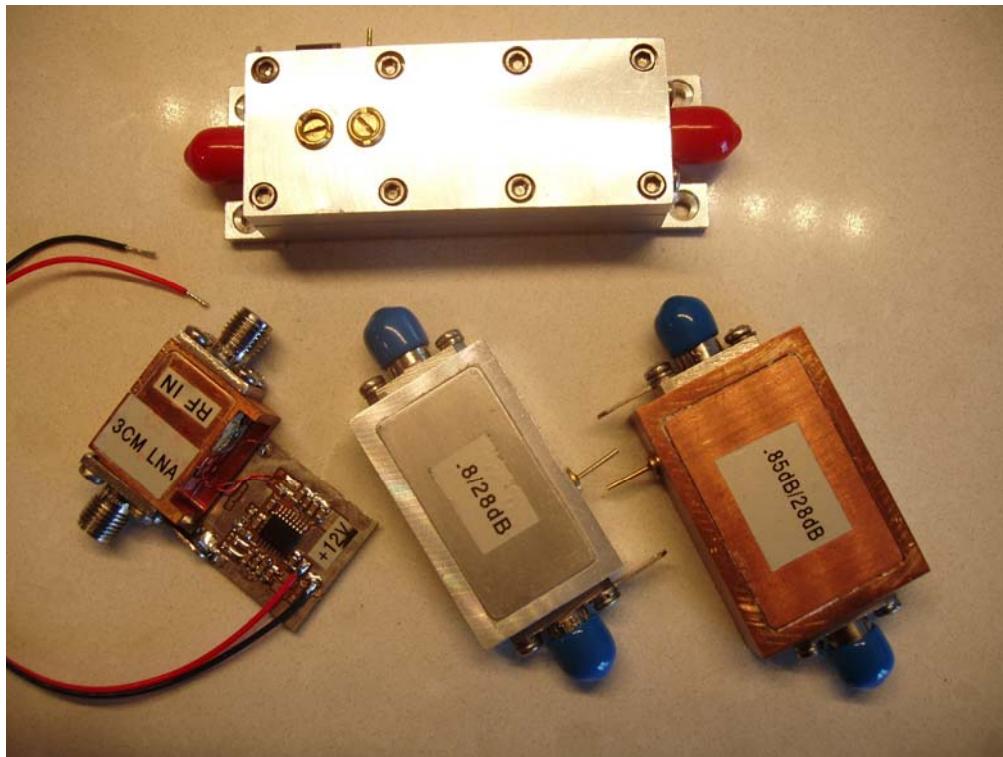

Critical construction and design points

- Ground plane connections, especially Source leads of GaAs FET, rf connector, and pcb ground plane to enclosure connection
- Input connector transition, connector quality
- Layout
- Bias circuit implementation
- Enclosure size, metal conductivity and connector attachments
- Preferred: Al, Cooper, Silver or Gold plated metals
- Components quality and size, smaller components are preferred
- Soldering
- For high frequency amplifiers, machining is necessary

Appendix – complex mathematics

COMPLEX ADDITION

To add two complex numbers, use either rectangular form **and** add their real **and** imaginary parts together, respectively:

$$(a+jb) + (c+jd) = (a+c) + j(b+d)$$

COMPLEX DIVISION

To divide two complex numbers, use polar format; then divide the magnitude of the numerator by the magnitude of the denominator **and** subtract the angle of the denominator from the angle of the numerator:

$$\frac{Z_1}{Z_2} = \frac{\rho_1 \angle \theta_1}{\rho_2 \angle \theta_2} = \frac{\rho_1}{\rho_2} \angle (\theta_1 - \theta_2)$$

COMPLEX SUBTRACTION


To subtract one complex number from another, use their rectangular form **and** subtract their real **and** imaginary parts, respectively:

$$(a+jb) - (c+jd) = (a-c) + j(b-d)$$



References

- Pozar M. David, 2005 Microwave Engineering ISBN 0-471-44878-8
- Maxim integrated, Application Note 3169, AN3169, Jul 08, 2004
- The ARRL UHF/Microwave Experimenters Manual, ISBN 10: 0972593126
- Chris Bowick, RF Circuit Design
- Joseph F. White, High Frequency Techniques
- Popovic Goran, 3cm LNA, MUD proceeding 2012, Santa Clara
- Fritz Dellsperger, Smith-Chart Software V4.1
- Complete RF Amplifier Design and Analysis Calculator,
- AWR Microwave Office V 14.03
- <https://www.microwaves101.com/encyclopedia/stability-factor>
- <https://www.daycounter.com/Calculators/Complete-RF-Amplifier-Design-Analysis-Calculator.phtml>

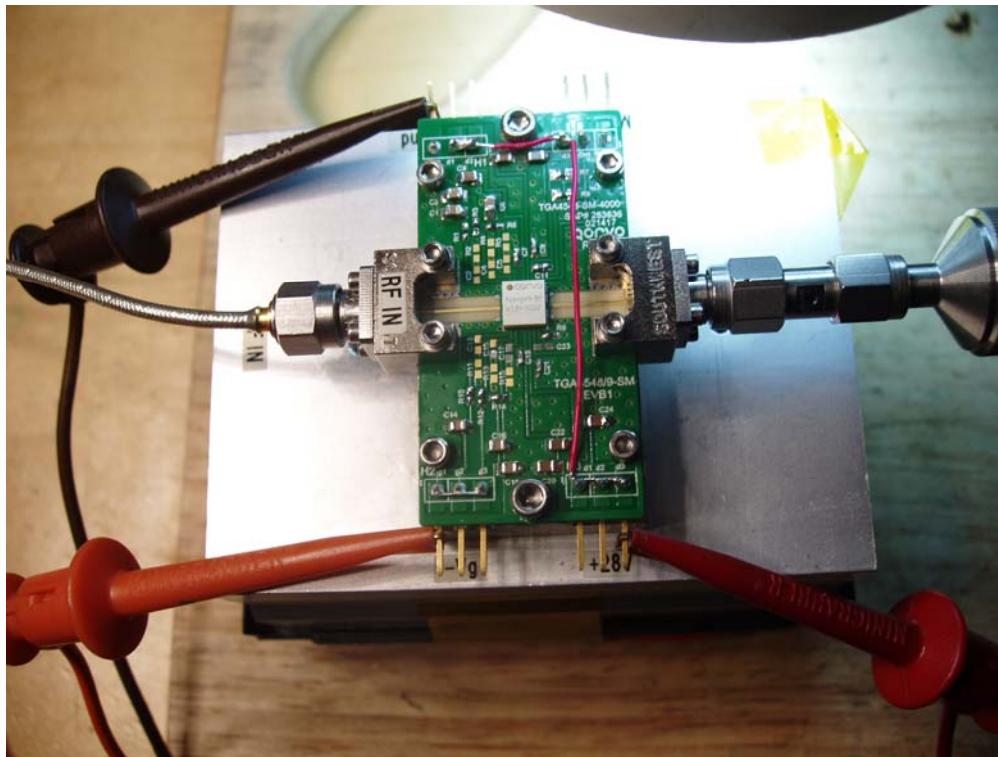Appendix: 10W 24GHz Power Amplifier with TGA4549 report



DC converter 12 to 28V/2.3A LM5122

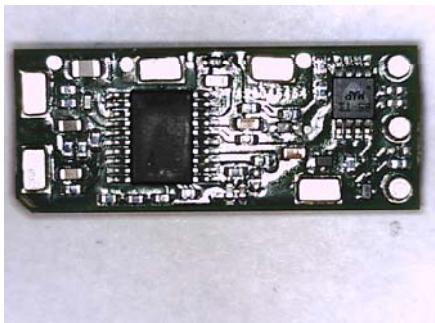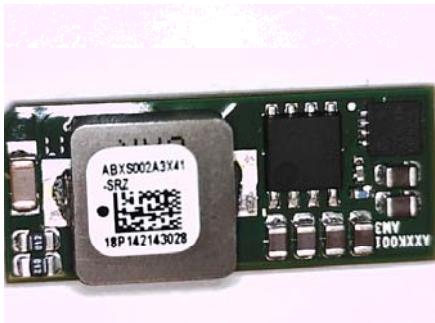


65W Boost Converter: Non-Isolated DC-DC Modules
8Vdc -16Vdc input; 16Vdc to 34Vdc output; 65W Output power (max.)



RoHS Compliant

Applications

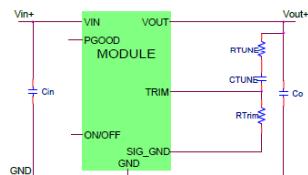- Industrial equipment
- Distributed power architectures
- Telecommunications equipment



Features

- Compliant to RoHS II EU "Directive 2011/65/EU"
- Compliant to IPC-9592 (September 2008), Category 2, Class II
- Compatible in a Pb-free or SnPb reflow environment (2 versions)
- Compliant to REACH Directive (EC) No 1907/2006
- Wide Input voltage range (8Vdc-16Vdc)
- Output voltage programmable from 16 to 34Vdc via external resistor
- Tunable Loop™ to optimize dynamic output voltage response
- Power Good signal
- Output overcurrent protection (non-latching)
- Over temperature protection
- Remote On/Off
- Ability to sink and source current
- Support Pre-biased Output
- Optimized for conduction-cooled applications
- Small size: 27.9 mm x 11.4 mm x 7.5 mm(MAX)
(1.1 in x 0.45 in x 0.295 in)
- Wide operating temperature range (-40°C to 85°C)
- UL® 60950-1 2nd Ed. Recognized, CSA¹ C22.2 No. 60950-1-07 Certified, and VDE¹ (EN60950-1 2nd Ed.) Licensed
- ISO** 9001 and ISO 14001 certified manufacturing facilities


Description

The Boost power modules are non-isolated dc-dc converters that can deliver up to 65W of output power. The module can operate over a wide range of input voltage ($V_{IN} = 8Vdc-16Vdc$) and provide an adjustable 16 to 34VDC output. The output voltage is programmable via an external resistor. Features include remote On/off, over current and over temperature protection. The module also includes the Tunable Loop™ feature that allows the user to optimize the dynamic response of the converter to match the load with reduced amount of output capacitance leading to savings on cost and PWB area.



First test results 😞



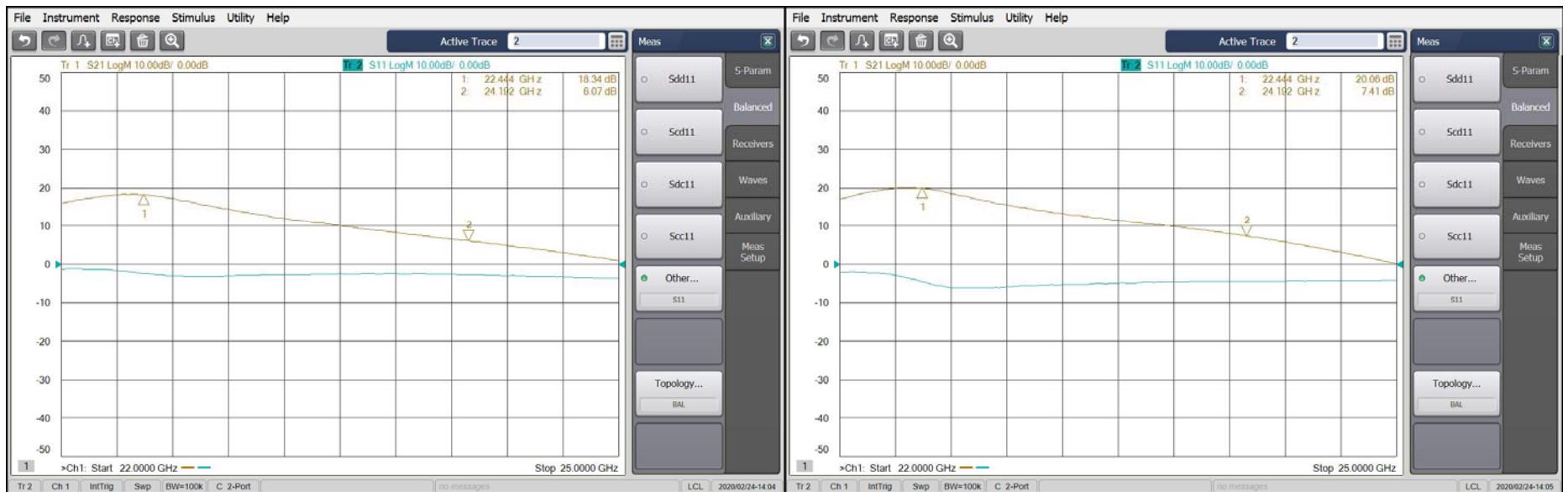Little better, but still poor performance



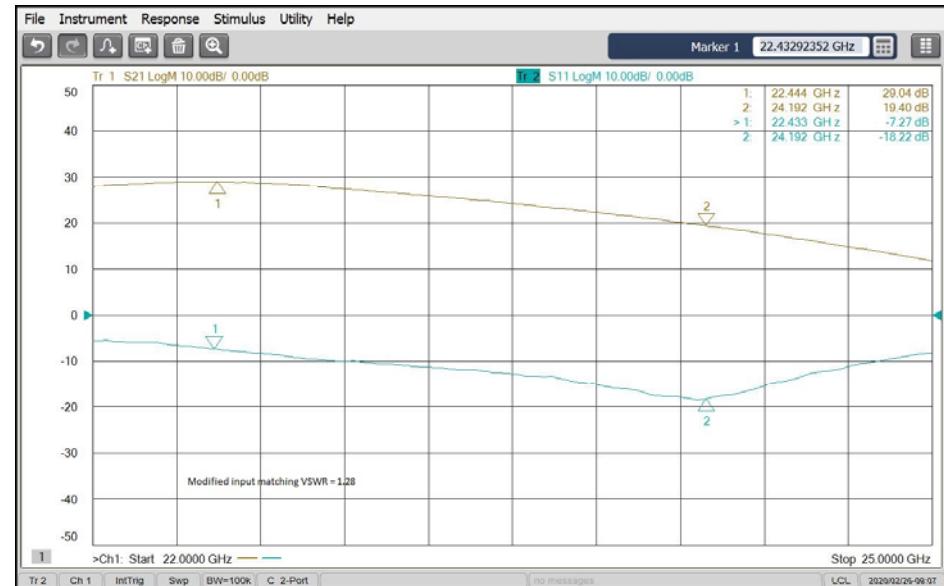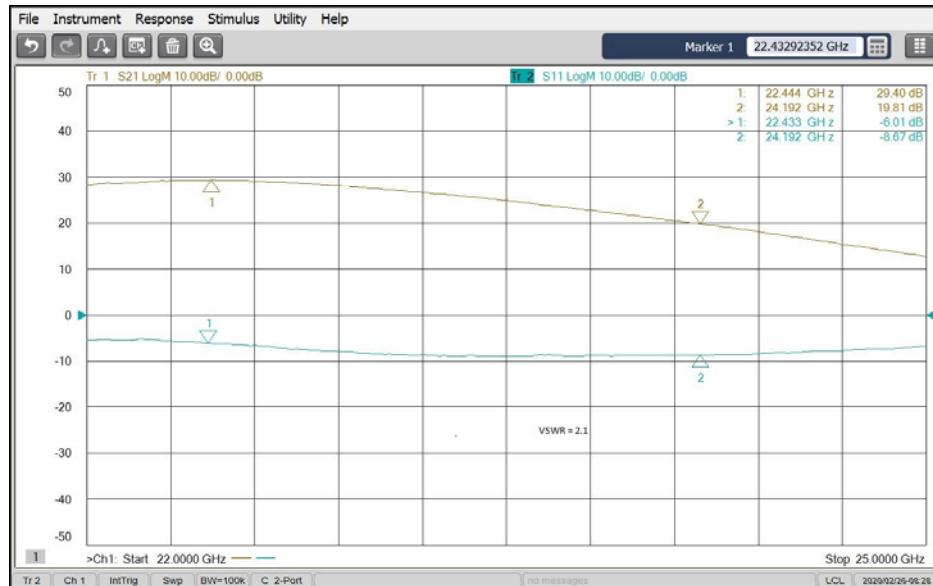Finally ☺ 100 mW in - 5.5 W out, 28V/1A
 max. input power 23dBm 200mW - no smoke



24GHz Output power, 19dBm in

