Cheap & Simple Transverters and Microwave Multiband

Paul Wade W1GHZ

902 MHz to 10 GHz



Cheap and Simple Transverters

- Design Philosophy Gain is Cheap
- Cheap MMICs for gain
- Ordinary capacitors and resistors
- Ordinary PC board material (FR4)
- Cheap SMA connectors from China (ebay)
- Cheap gain makes up for losses
- Printed Filters Magic is in PC Board
- Pipe-cap Filters cheap and readily available
- - Goal: > \$100 per band
- Add bits for higher performance

Transverter Updates

- New MMICs
 - Higher gain and power
 - Lower Noise Figure
 - New footprint SOT-89 package
- Synthesizer for LO
 - No multipliers, except 5.7 & 10 GHz
 - Frequency accuracy
- Soldermask protect filters, ease assembly

902 MHz - soldermask



1296 – soldermask, new MMICs



Hairpin Filter with Soldermask

2304 & 3456 MHz TRANSVERTER

2304 or 3456 MHz

Pipe-cap Filters

5760 Transverter

10 GHz Transverter

Six identical amplifiers

Local Oscillator

- Synthesizer
 - Flexible frequency for Multiband
- Cheap ones go to 4 GHz
 - ADF4350, ADF4351
 - Need Multplier for 5 & 10 GHz
- DigiLO to 6GHz
- ADF5355 to 13 GHz
- DB6NT \$\$

LO – Cheap Chinese Synthesizer

ADF4350 Board+ 137Mhz-4.4G RF source Sweep Phase Locked^{***} Loop Board+12864 Display \$65.25

Signal source 10 GHz/ 24 GHz

 \circ 1, measuring power range-45~-5 dBm (external RF attenuator can be extended to 80dBm)

o2, the measurement resolution of 0.1 dBm power

o3, measurement frequency range 1 1MHz-5GHz

04, the measured power 1nW ~ 2W
05, the working voltage of 5VDC
(direct selection MICRO-USB
powered)

o6, the working current <50 mA

- o7, the working temperature of -40 °C
- ~ 65 °C degrees Celsius

○8, storage temperature -40 °C ~ 65
°C degrees Celsius

o9, size 50 * 50 * 25 mm length X

3456 MHZ Lunch Box Transverter

ADF4350

Better ADF4351

Local Oscillator - digiLO

SDMG Group Transverter

- Control ADF4350 with Arduino
- Multiple transverter boards
- Select band and LO frequency with Arduino
- Group build
- Add bands as desired

Synthesizer on Arduino, 10 GHZ Multiplier, by Drew, N7DA

Sequencer + IF interface

IF interface – PIN diode switch RF on the PCB backside

What else could Arduino do?

- Load Synthesizer Frequency
- Inhibit Transceiver output
- VSWR monitor and shutdown

 analog inputs
- Monitor voltage
- Temperature monitor (external sensor)
- TR relay auxiliary contacts
- Latching relay driver
- Multiband transmit protection (Rover)

Coax Relay

ON – High Power – High Isolation

SWITCHING

- Low Power
- Low Isolation
- Easily damaged

Waveguide Switches

- High Power and Isolation
- but NOT while switching

Solid-state switch

HMC849 RF Switch Module Single-Pole Double-Throw

Buy It Now

Add to cart

DISCOVER

Switch for Multiband LO

HMC252 DC to 3GHz Non-reflective Single Pole Six Throw

Buy It Now

View Cart

Make Offer

DISCOVER

Longtime member

FT-817 with Panadapter

SDR

- Several wideband SDR available
- Good receiver
- Clean transmit a problem
- Simple matter of software...
- Better as test equipment? satsagen

Hermes Lite SDR

Get it on the air!

More Details

www.w1ghz.org

Arduino sketches (software)

• Pictures, schematic, parts list, etc.

• Boards are available